


## Experiment 1

**Objective:**

**Determination of unknown capacitance using De Sauty's Bridge method.**

**Items Required:**

1. De Sauty's Bridge Trainer
2. 2mm Patch cords
3. Multimeter

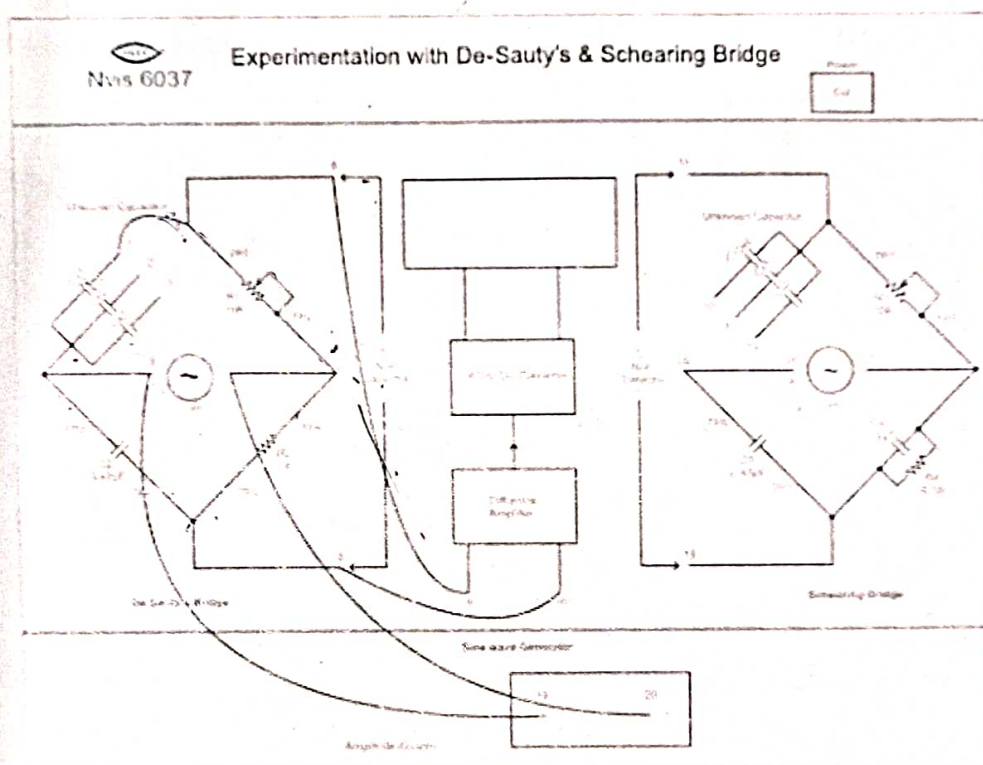**Procedure:**

1. Connect mains cord to the Trainer.
2. Connect terminal 1 to 4 (for evaluating unknown capacitance  $C_{x1}$ ).
3. Rotate variable resistance  $R_1$  towards anticlockwise direction.
4. Connect null detector (i.e. terminal 5 to 9 and 8 to 10).
5. Set Amplitude Control knob in fully clockwise direction.
6. Connect terminal 19 to 6 and 20 to 7.
7. Now switch 'On' the power supply.

8. Now vary the **R1** towards clockwise direction very precisely until the Null Point is detected.
- (Null Point: It is the point where the voltage is minimum and on rotating **R1** in any direction voltage always increases.)
9. Now remove the patch cord between terminal 1 & 4 and record the value of **R1** in the observation table using multimeter.
10. Repeat above procedure for different value of unknown capacitors (i.e. **Cx2** and **Cx3**).
11. Tabulate all the retrieved data in observation table below.

Observation Table:

S. No.	Unknown Capacitor	Resistance R1 ohm	Resistance R2 ohm	Capacitor C2 μF
1.	Cx1			
2.	Cx2			
3.	Cx3			

Actual  
 0.1 μF  
 0.22 μF  
 0.47 μF

Calculations

1. For unknown Capacitance Cx1:

$$C_{X1} = R_2 \times \frac{C_2}{R_1}$$

$$= 2.311 \mu F$$

0.08499 μF

2. For unknown Capacitance Cx2:

$$C_{X2} = R_2 \times \frac{C_2}{R_1}$$

$$= 0.944 \mu F$$

0.2078 μF

3. For unknown Capacitance Cx3:

$$C_{X3} = R_2 \times \frac{C_2}{R_1}$$

$$= 0.4324 \mu F$$

0.4936 μF

$\frac{1.0K}{5.7K} \times 0.07 \mu F$   
 0.01228 μF  
 0.824 μF