

Objective:


Determination of unknown inductance using Maxwell's inductance bridge method

Equipments Needed:

1. Nvis 6533
2. 2 mm patch cords
3. Digital multimeter
4. Oscilloscope

Circuit diagram:

Mimic illustration with connections for Maxwell's inductance bridge method for measurement of unknown inductance is shown in the below figure.

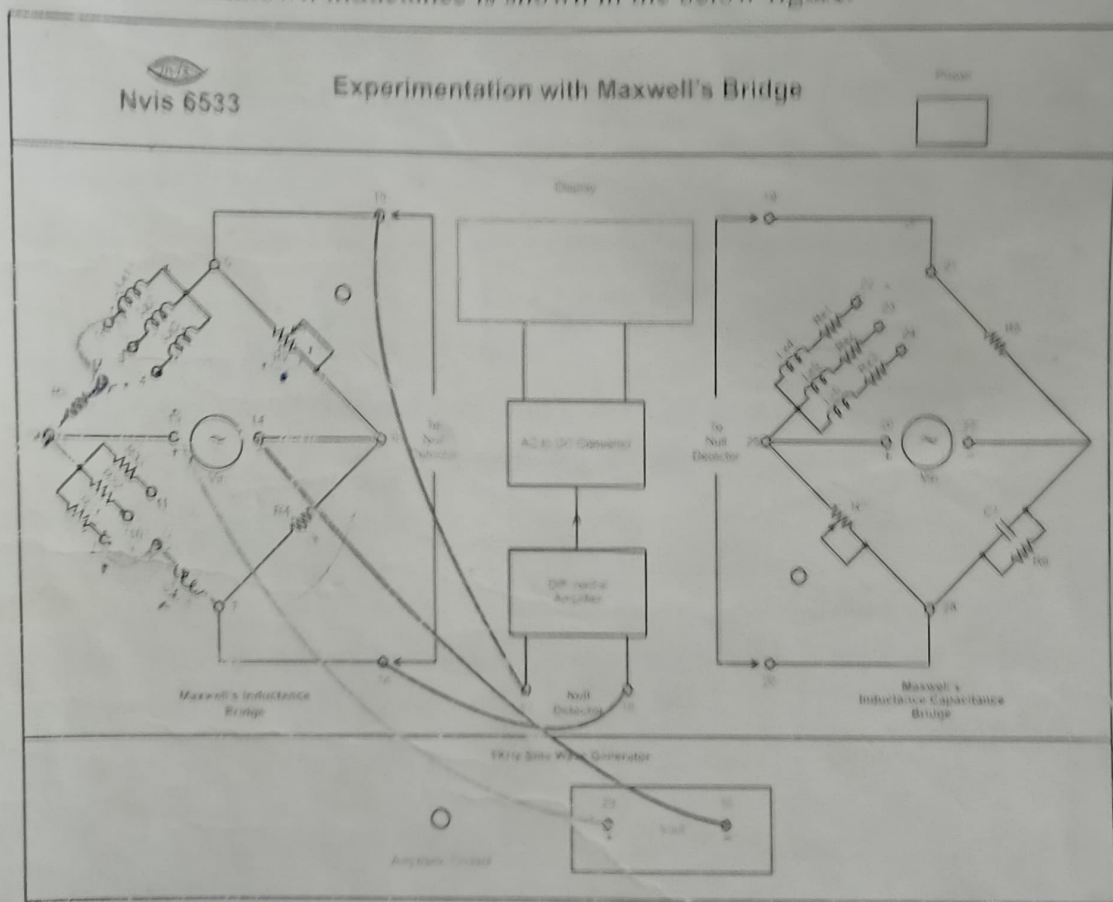
**Procedure:**

1. Connect a patch cord between socket '13' of V_{in} terminals of Maxwell's inductance bridge and socket '29' of V_{out} terminals of the 1 KHz sine wave generator.

Observation Table 2:

R_2 Ω	R_4 Ω	$R_3 = R_{32}$ Ω	L_1 μH	$L_{x2} = L_1.R_2/R_4$ μH	$R_x = R_2.R_3/R_4$ Ω

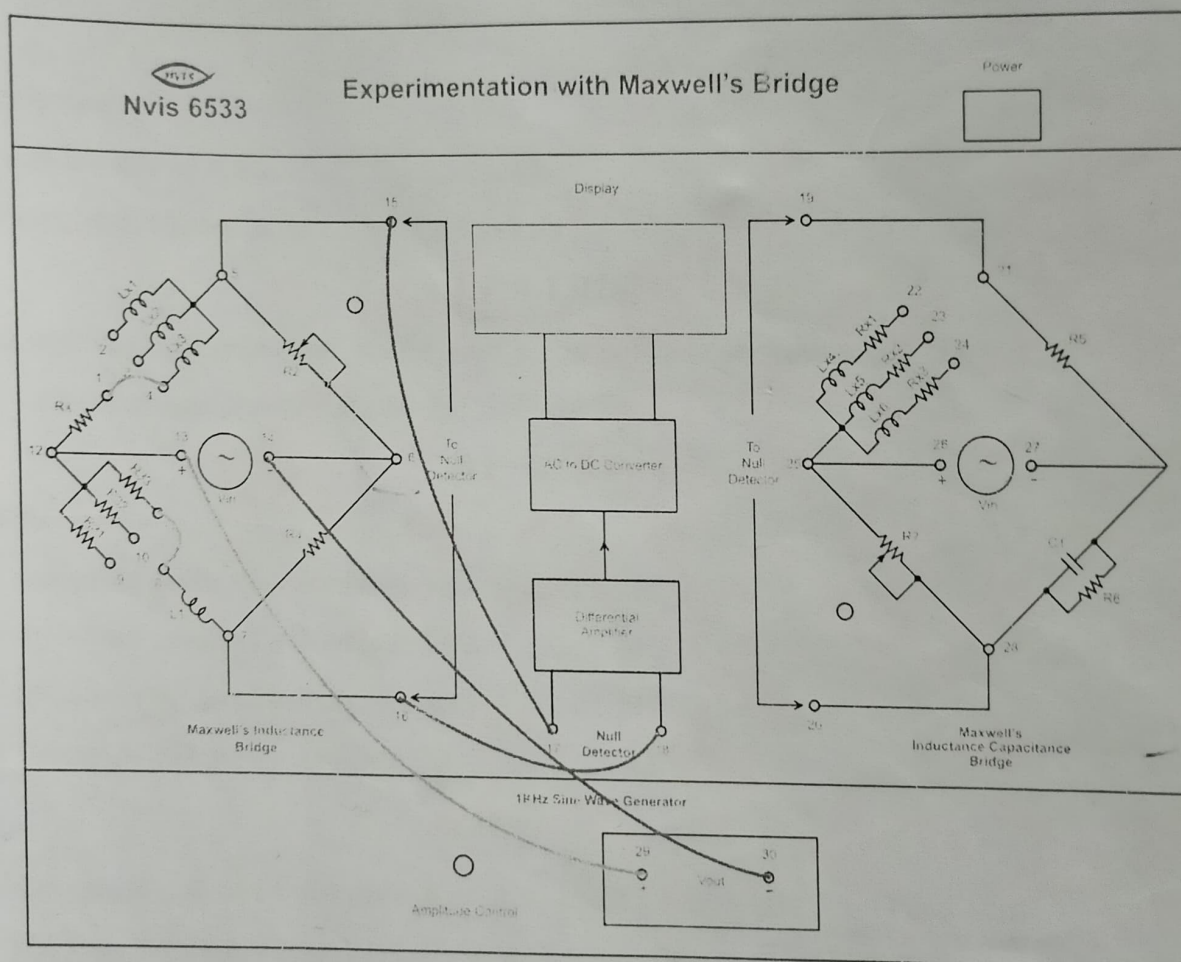
20. Now connect a patch cord between sockets '1' and '4' and another patch cord between sockets '8' and '11' as shown in below figure to determine the value of L_{x3} and R_{x3} .



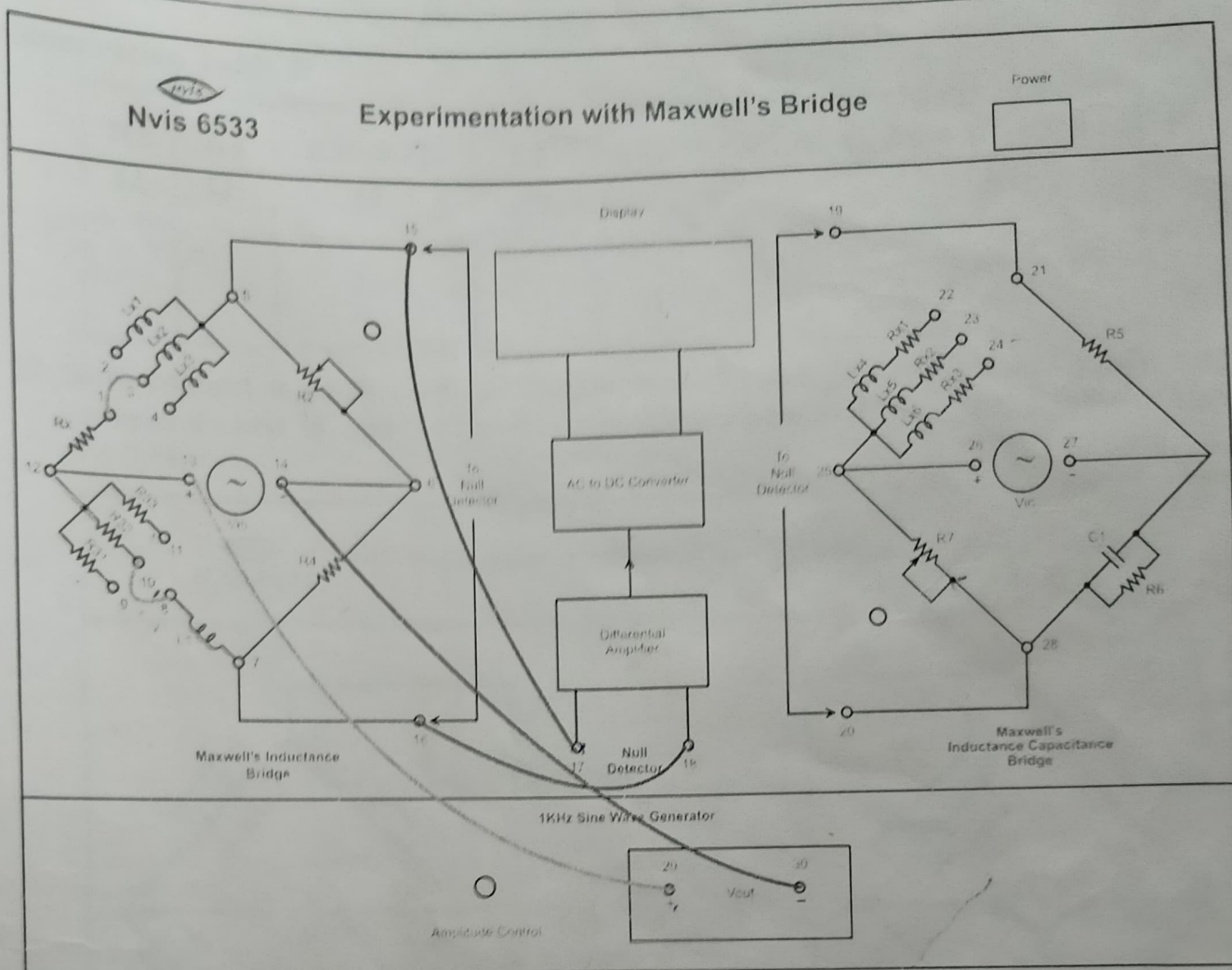21. Now repeat the above procedure from step 6 to 9.
22. Remove all the patch cords connected to bridge circuit for accurate reading of R_2 .
23. Now Measure the resistance R_2 between test-points '5' and '6' using a digital multimeter.
24. Calculate the value of inductance L_{x3} and resistance R_x using the formula

$$L_x = \frac{L_1.R_2}{R_4}$$

Where, $L_x = L_{x3}$, $L_1 = 12\mu H$, $R_4 = 100\Omega$



15. Repeat the above procedure from step 6 to 9.
16. Remove all the patch cords connected to bridge circuit for accurate reading of R_2 .
17. Now measure the value of resistance R_2 between test-points '5' and '6' using a digital multimeter.
18. Calculate the value of inductance L_{x2} and resistance R_x using the formula

$$L_x = \frac{L_1 \cdot R_2}{R_4}$$

Where, $L_x = L_{x2}$, $L_1 = 12\mu\text{H}$, $R_4 = 100\Omega$

19. Calculate the value of unknown resistance using the formula

$$R_x = \frac{R_2 \cdot R_3}{R_4}$$

Where, $R_3 = 237\Omega$, $R_4 = 100\Omega$

2. Connect a patch cord between socket '14' of Vin terminals of Maxwell's inductance bridge and socket '30' of Vout of the 1 KHz sine wave generator.
3. Connect a patch cord between sockets '1' and '2' and connect another patch cord between sockets '8' and '9' to determine the value of L_{x1} and R_{x1} .
4. Connect patch cords between sockets '15' and '17' and sockets '16' and '18' for the purpose of null detection.
5. Set the potentiometer R_2 in counter clockwise direction.
6. Switch 'On' the power supply.
7. Set the amplitude of 1 KHz sine wave generator maximum i.e. rotate amplitude control knob fully clockwise.
8. Rotate the potentiometer R_2 towards clockwise direction very precisely to find a condition where null (Zero or minimum reading) is displayed on DPM.
9. Switch 'Off' the power supply.
10. Remove all the patch cords connected to bridge circuit for accurate reading of R_2 .
11. Now measure the resistance R_2 between test-points '5' and '6' using a digital multimeter.
12. Calculate the value of inductance L_{x1} and resistance R_x using the formula

$$L_x = L_1 \cdot R_2 / R_4$$

Where, $L_x = L_{x1}$, $L_1 = 12 \mu H$, $R_4 = 100 \Omega$

13. Calculate the value of unknown resistance using the formula

$$R_x = R_2 \cdot R_3 / R_4$$

Where, $R_3 = 120 \Omega$, $R_4 = 100 \Omega$

Observation Table 1:

R_2 Ω	R_4 Ω	$R_3 = R_3$ Ω	L_1 μH	$L_{x1} = L_1 \cdot R_2 / R_4$ μH	$R_x = R_2 \cdot R_3 / R_4$ Ω

14. Now again connect a patch cord between sockets '1' and '3' and another patch cord between sockets '8' and '10' as shown in below figure to determine the value of L_{x2} and R_{x2} .

25. Calculate the value of unknown resistance using the formula

$$R_x = R_2.R_3 / R_4$$

Where, $R_3=470\Omega$, $R_4=100\Omega$

Observation Table 3:

R_2 Ω	R_4 Ω	$R_3 = R_3$ Ω	L_1 μH	$L_{x3} = L_1.R_2/R_4$ μH	$R_x = R_2.R_3/R_4$ Ω

Calculation:

Measured value of R_2 is. Ω .

Now calculate the value of L_x by the formula

$$L_x = L_1.R_2/R_4$$

Measured value of resistance R_x by multimeter between sockets Ω .

Now calculate the values of R_x by the formula

$$R_x = R_2.R_3/R_4$$

Result:

The unknown value of inductance $L_{x1} = \dots\dots\dots\mu H$.

The unknown value of inductance $L_{x2} = \dots\dots\dots\mu H$.

The unknown value of inductance $L_{x3} = \dots\dots\dots\mu H$.

The unknown value of resistance $R_x = \dots\dots\dots\Omega$.

Note:

1. The actual values of inductors L_{x1} , L_{x2} and L_{x3} are 56 μH , 24 μH and 12 μH .
2. The actual value of resistor R_x is 470 Ω .
3. Calculated R_x is $(R_x + r)$, where r is internal resistance of corresponding inductor.
4. Small amount of error would be there due to component tolerance and also due to human error.